

## Dipôles passifs

$$18) a) P = U \cdot I \Rightarrow I = \frac{P}{U} = \frac{75 \text{ W}}{220 \text{ V}} = 0,341 \text{ A}$$


$$R = \frac{U}{I} = 645 \Omega$$

$$b) U = 25 \text{ V} \quad I = 0,120 \text{ A}$$

$$R = 208,33 \Omega \quad P = U \cdot I = 3 \text{ W}$$

c) Si la puissance augmente  $3 \text{ W} \rightarrow 75 \text{ W}$   
le filament devient plus chaud et la  
résistance augmente  $208 \Omega \rightarrow 645 \Omega$

19)

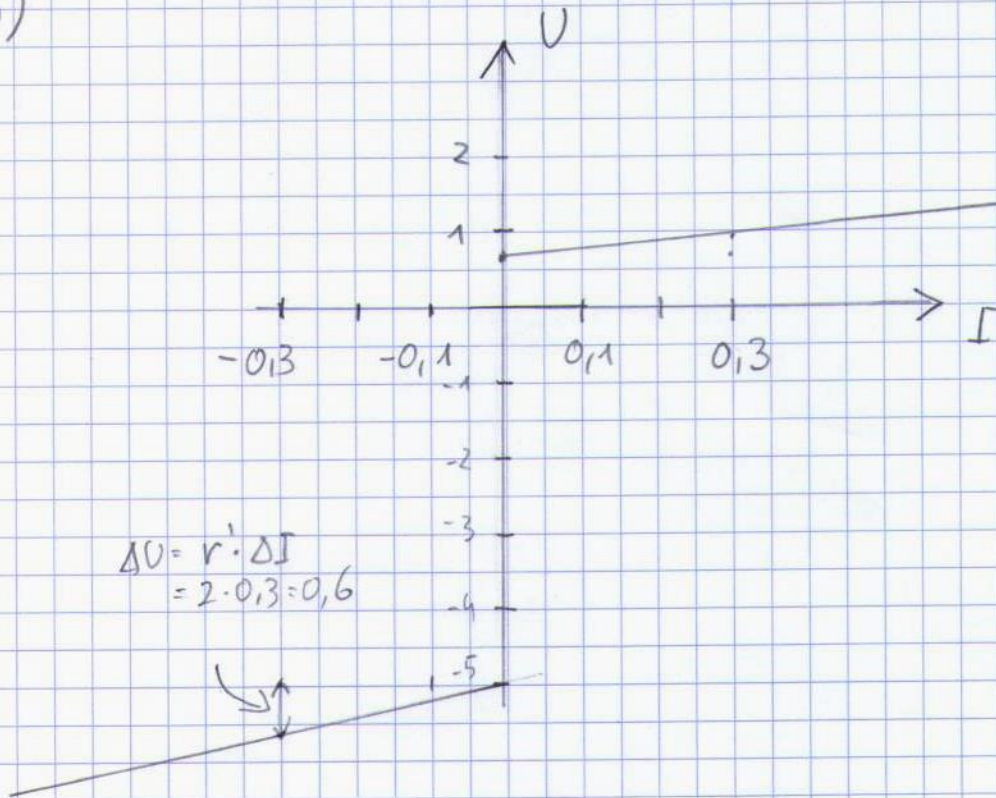

$$\Delta U = r' \cdot \Delta I$$

$$= 2 \cdot 0,3 = 0,6$$

$$20) R_{\text{Fe}} = 10 \cdot 10^{-8} \cdot \frac{\text{L}}{S} = 6,416 \Omega \quad R_{\text{Cu}} = 1,7 \cdot 10^{-8} \frac{\text{L}}{S} = 1,1 \Omega$$

$$S = \frac{\pi}{4} \cdot d^2 = 3,1415 \cdot 10^{-8} \text{ m}^2$$

$$21) a) I_1 = \frac{P}{U_1} = \frac{2000}{110} = 18,18 \text{ A} \quad I_2 = \frac{P}{U_2} = 0,0909 \text{ A}$$

Perte par effet Joule sur  $R = 5 \Omega$


$$P_1 = R \cdot I_1^2 = 1652 \text{ W}$$

(82% de 2000 W)

$$P_2 = R \cdot I_2^2 = 0,041 \text{ W}$$

(0,002%)

22)

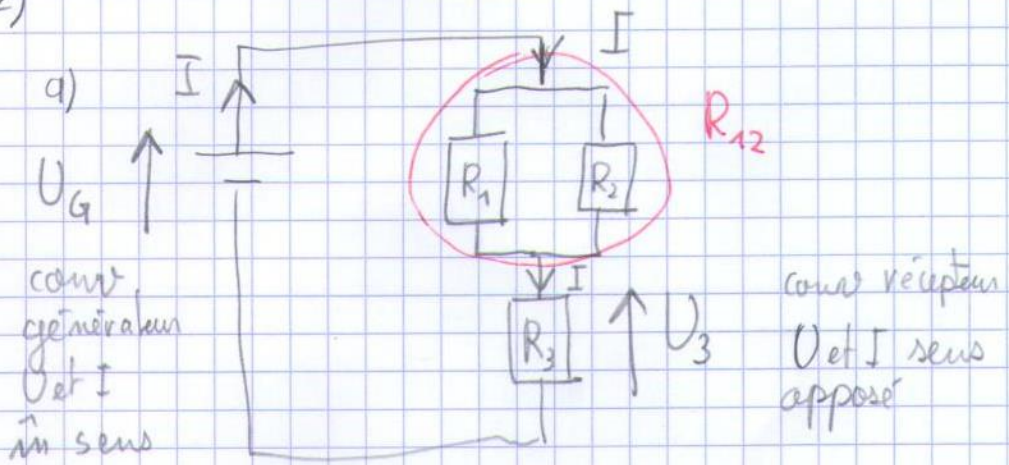

$$a) R_{12} = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = 66,67 \Omega$$

$$R_{\text{tot}} = R_{12} + R_3 = 116,67 \Omega$$

b) Courant total:  $I = \frac{U_G}{R_{\text{tot}}} = 0,1714 \text{ A}$

c) Tension  $U_3 = R_3 \cdot I = 8,57 \text{ V}$

Tension  $U_1 = U_2 = U_G - U_3 = 11,43 \text{ V}$

Courant  $I_1 = \frac{U_1}{R_1} = 0,1143 \text{ A}$

23) conducteur haute tension

a)  $R = \rho \cdot \frac{L}{S} = 1,7 \cdot 10^{-8} \cdot \frac{12000}{630 \cdot 10^{-6}} = 0,324 \Omega$

b) pour  $I = 5000 \text{ A}$   $\Delta U = R \cdot I = 1619 \text{ V}$

c) Puissance totale:  $P = U \cdot I = 75 \text{ MW}$

Puissance perdue:  $P_{\text{Joule}} = R \cdot I^2 = \Delta U \cdot I = 8,1 \text{ MW}$   
10% perte thermique